

Solutions to Sheet 5

1. LRC circuit, no external potential

(i) Rewrite the first two relations as $I(t) = -\dot{Q}(t) = -C \dot{U}(t)$, and find $U(t) = -LC \ddot{U}(t) - RC \dot{U}(t) \Rightarrow \ddot{U}(t) + \frac{R}{L} \dot{U}(t) + \frac{1}{LC} U(t) = 0$.

(ii) This is a linear and homogeneous differential equation.

(iii) $R = 0$: $\ddot{U}(t) + \frac{1}{LC} U(t) = 0$. If $U(t) = e^{izt}$, $z^2 = \frac{1}{LC} \Rightarrow z_{1,2} = \pm \frac{1}{\sqrt{LC}}$. Thus $U_{1,2}(t) = \exp\left(\pm \frac{i}{\sqrt{LC}} t\right)$.

(iv) Clearly, with $\omega = \frac{1}{\sqrt{LC}}$, $U_{1,2} = \exp(\pm i \omega_0 t) = \cos(\omega_0 t) \pm i \sin(\omega_0 t)$. Since the general solution is a linear superposition of these two, we can have any combination of sines and cosines $\Rightarrow U(t) = A \cos(\omega_0 t) + B \sin(\omega_0 t)$.

(v) $U(t) = e^{izt}$, $-z^2 + i \frac{R}{L} z + \frac{1}{LC} \Rightarrow z_{1,2} = \pm i \frac{R}{2L} \pm \frac{1}{2} \sqrt{-\frac{R^2}{L^2} + \frac{4}{LC}}$. If $R^2/L^2 < 4/(LC)$ (i.e.,

$R < 2 \sqrt{L/C}$) the square root is real, and we have, with α and ω as on the sheet, $z_{1,2} = i \alpha \pm \omega$.

(vi) $U_{1,2} = \exp(-\alpha t \pm i \omega t)$
 $= \exp(-\alpha t) \exp(\pm i \omega t) = \exp(-\alpha t) (\cos(\omega t) + i \sin(\omega t))$

In the same way as in 4, the real solution is thus a superposition of $\exp(-\alpha t) \cos(\omega t)$ and $\exp(-\alpha t) \sin(\omega t)$,

$U(t) = \exp(-\alpha t) (A \cos(\omega t) + B \sin(\omega t))$.

(vii) If $R = 0$, $\alpha = 0$ and $\omega = \omega_0$, so we trivially find the requested result.

2. LRC circuit, sinusoidal potential

(i) Trivial differentiation, plus substitution of $I(t) = -\dot{Q}(t)$.

(ii) The equation (2) is linear and inhomogeneous.

(iii) $(-\Omega^2 L + i \Omega R + 1/C) I_0 e^{i \Omega t} = \Omega V_0 e^{i \Omega t}$, or

$$I_0 = \frac{\Omega V_0}{(-\Omega^2 L + i \Omega R + 1/C)} = \frac{V_0(-\Omega L + 1/(\Omega C) - i R)}{(-\Omega L + 1/(\Omega C) + i R)(-\Omega L + 1/(\Omega C) - i R)} = \frac{V_0(-\Omega L + 1/(\Omega C) - i R)}{(-\Omega L + 1/(\Omega C))^2 + R^2}.$$

(iv) $I_0 = \frac{V_0(-\Omega L + 1/(\Omega C) - i R)}{(-\Omega L + 1/(\Omega C))^2 + R^2}$. $|I_0| = \frac{V_0}{\sqrt{(-\Omega L + 1/(\Omega C))^2 + R^2}}$, $\phi = \arg(I_0) = \text{atan}\left(\frac{R}{-\Omega L + 1/(\Omega C)}\right)$

(v) a) taking the complex conjugate of the auxiliary equation, we must show that

$(\dot{I}(t))^* = \frac{d}{dt} (I(t)^*)$. This is straightforward once we realise that t is real, so that

$$(I(t))^* = \left(\lim_{h \rightarrow 0} \frac{I(t+h) - I(t)}{h} \right)^* = \lim_{h \rightarrow 0} \frac{I(t+h)^* - I(t)^*}{h} = \frac{d}{dt} (I(t)^*).$$

b) Adding the equation and its complex conjugate we get the desired answer.

(vi) Trivially true! If $R = 0$, $\phi = 0$, and the phase difference is 90° .

3.


(i) take $y(x) = \exp(i z x)$: $-z^2 = -12$, $z = \pm \sqrt{12}$: $y(x) = A \cos(\sqrt{12} x) + B \sin(\sqrt{12} x)$.

(ii) take $y(x) = \exp(i z x)$: $-z^2 + i z + 12 = 0$, $z = -\frac{1}{2} i \pm \frac{1}{2} \sqrt{-1 + 48}$:



$$y(x) = \exp\left(\frac{1}{2} x\right) \left(A \cos(\sqrt{47/4} x) + B \sin(\sqrt{47/4} x) \right).$$

4.

(i)

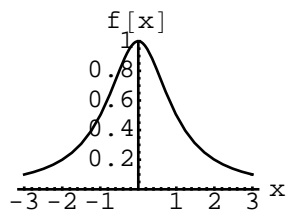

(ii)

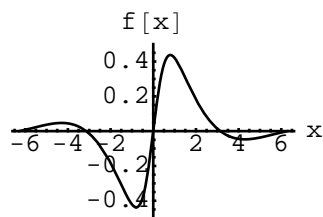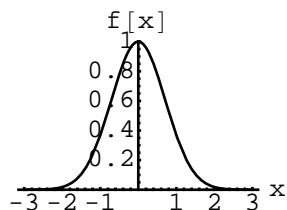

5.

(i) $e^{i 3 \pi/2}$

(ii) $2 e^{-i \pi/3}$

(iii) $(2 e^{i \pi/3})^{1/4} = 2^{1/4} e^{i \pi/12}$

(iv) One solution $(2 e^{-2 i \pi/3})^{1/4} = 2^{1/4} e^{-i \pi/6}$. Other solutions differ by phase by $2 \pi/4 = \pi/2$,

$$z = 2^{1/4} e^{-i 2 \pi/3}, 2^{1/4} e^{-i \pi/6}, 2^{1/4} e^{i \pi/3}, 2^{1/4} e^{i 5 \pi/6}.$$

6.

(i) Substitute: $-9 C e^{i3x} + 4 C e^{i3x} = 2 e^{i3x}$; $C = -2/5$.

(ii) General solution of the homogeneous equation $y(x) = A e^{i2x} + B e^{-i2x}$. Solution to inhomogeneous problem: $y(x) = A e^{i2x} + B e^{-i2x} - \frac{2}{5} e^{i3x}$. $y(0) = 0$, $y'(0) = 0$:

$$A + B - \frac{2}{5} = 1, i \left(2A - 2B - \frac{6}{5} \right) = 0.$$

Solution: $A = 1$, $B = \frac{2}{5}$.

$$y(x) = e^{i2x} + \frac{2}{5} e^{-i2x} - \frac{2}{5} e^{i3x}.$$