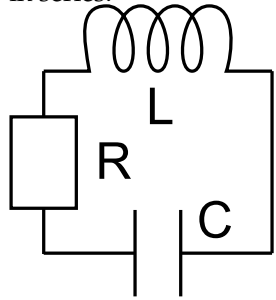


## P201 Workshop 5, Week 5

Please follow the instructions of your supervisor regarding timing of these problems.

### Physics

1. Consider a closed circuit with a resistor  $R$ , an inductor  $L$ , and a capacitor  $C$  in series.




The time-dependent charge  $Q(t)$  on the capacitor, the corresponding voltage drop across the capacitor  $U(t)$ , and the current  $I(t)$  through the circuit are related by  $Q(t) = CU(t)$  and  $I(t) = -\dot{Q}(t)$ . Furthermore, the voltage  $U(t)$  must be equal to the sum of the voltages  $L\dot{I}(t)$  (inductor) and  $RI(t)$  (resistor), i.e.,  $U(t) = L\dot{I}(t) + RI(t)$

- (i) Use these two equations to eliminate the charge  $Q(t)$  and the current  $I(t)$  in order to find a differential equation for  $U(t)$ . Show that this differential equation reads

$$\ddot{U}(t) + \frac{R}{L}\dot{U} + \frac{1}{LC}U(t) = 0. \quad (1)$$

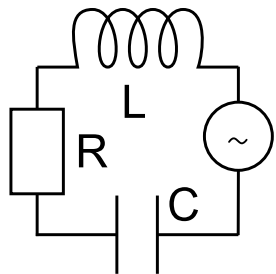- (ii) Classify (1) (as nonlinear/linear, homogeneous or inhomogeneous).  
 (iii) Find two independent solutions of (1) for the special case of zero resistance,  $R = 0$  (insert  $\exp(izt)$  and find possible values for  $z$ ).  
 (iv) Show that the general solution can be written as  $U(t) = [A \cos(\omega_0 t) + B \sin(\omega_0 t)]$  with  $\omega_0 = \sqrt{1/LC}$ .  
 (v) Now find two independent solutions of (1) for the general case,  $R \neq 0$ , (insert  $\exp(izt)$  and find possible values for  $z$ ). Assume that  $R < 2\sqrt{L/C}$ .  
 (vi) Show that the general solution can be written as  $U(t) = e^{\alpha t}[A \cos(\omega t) + B \sin(\omega t)]$  with  $\alpha = R/(2L)$ ,  $\omega = \sqrt{1/(LC) - R^2/(4L^2)}$ .  
 (vii) Show that this solution is consistent with your solution in part 3.



Consider the same  $RLC$  circuit, but now with an external voltage  $V(t) = V_0 \sin(\Omega t)$ ,  $V_0 > 0$  applied. The voltage  $V(t)$  must fulfill  $L\dot{I}(t) + RI(t) = Q(t)/C + V(t)$ , where  $I(t)$  is the time-dependent current through the circuit.

2. (i) Find the differential equation for  $I(t) = -\dot{Q}(t)$  (hint: differentiate the

equation for the voltage),

$$L\ddot{I}(t) + R\dot{I}(t) + \frac{1}{C}I(t) = \Omega V_0 \cos(\Omega t). \quad (2)$$

- (ii) Classify (2) (as nonlinear/linear and homogeneous/inhomogeneous).  
 (iii) Consider the 'auxiliary' differential equation to (2), where  $\cos(\Omega t) = \text{Re}(e^{i\Omega t})$  is replaced by  $e^{i\Omega t}$ ,  $L\dot{I}^a(t) + RI^a(t) + I^a(t)/C = \Omega V_0 e^{i\Omega t}$ , and solve this equation by inserting  $I^a(t) = I_0 e^{i\Omega t}$  and determine  $I_0$ .  
 (iv) Calculate the polar form of the complex number  $I_0 = |I_0|e^{i\phi}$  (note that  $V_0 > 0$  is real!),  
 (v) \* Prove the following: a) If the complex current  $I^a(t)$  is a solution of the auxiliary equation, the complex conjugate  $[I^a(t)]^*$  is a solution of the same equation, with  $e^{i\Omega t}$  replaced by  $e^{-i\Omega t}$ , and b) consequently, the 'true' current  $I(t) = \text{Re}(I^a(t))$  is a solution of (2).  
 (vi) Use the polar form of  $I_0$  to find the 'true' current  $I(t) = \text{Re}(I^a(t)) = \text{Re}(I_0 e^{i\Omega t}) = |I_0| \cos(\Omega t + \phi)$ , i.e. the solution of (2). What is the value of  $\phi$  in the case  $R = 0$  (zero resistor), and what is the phase shift between the current  $I(t)$  and the voltage  $U(t)$  in that case?

### Math Practise

3. Find the general solution of  
 (i)  $y''(x) + 12y(x) = 0$ ; (ii)  $y''(x) + y'(x) + 12y(x) = 0$ .  
 4. Sketch the following curves  
 (i)  $f(x) = 1/(1+x^2)$ , (ii)  $f(x) = e^{-x^2}$ , (iii)  $f(x) = \sin(x)/(1+x^2)$ .  
 5. Find the polar form for the following complex numbers:  
 (i)  $-i$ , (ii)  $1 - \sqrt{3}i$  (iii)  $(1 + \sqrt{3}i)^{1/4}$ .  
 (iv) Find all solutions to  $z^4 = (-1 - \sqrt{3}i)$  (Hint: write in polar form.)

### Math Problems

6. (i) Consider the differential equation  $y''(x) + 4y(x) = 2e^{i3x}$ . Write a particular solution  $y_p(x)$  of this inhomogeneous equation as  $y_p(x) = Ce^{i3x}$  and determine the constant  $C$ .  
 (ii) \* Determine the general solution of this differential equation, and solve it for  $y(0) = 1, y'(0) = 0$ .

Reading for next week: FM, Chap. 15